
	Academic Year:	2022/2023	Term:	First term	
	Course Code:	Eective1	Course Title:	VLSI	

Cairo University
Faculty of Engineering
Electronics and Communications Engineering Department –
4th Year

VLSI PROJECT

Name	Sec	BN
عبدالمنعم احمد عبدالمنعم سلام	2	50
منى منصور امين محمد	4	30

Table of Contents

1- Layout of the basic cells	1
2- Layout of the multiplier core	2
3-Extract and simulation of the multiplier core.....	3
3.1 Case x=11111,y=111111 then p=000000000001.....	3
3.2 Case x=01111,y=100000 then p=110001000000.....	3
4-Performance estimation.....	4
4.1 Worst Case delay calculation.....	4
4.2 Max Frequency Calculation.....	4
4.3 Dynamic Power at max Frequency Calculation.....	4
4.4 Core area.....	4
5- Layout of the multiplier core after pads	5
6-Extract and simulation of the multiplier core after pads.....	6
6.1 Case x=01111,y=0111111 then p=001110110001.....	6
6.2 Case x=01111,y=100000 then p=110001000000.....	6
7-Performance estimation after pads.....	7
7.1 Worst Case delay calculation.....	7
7.2 Max Frequency Calculation.....	7
7.3 Dynamic Power at max Frequency Calculation.....	7

1-Layout of the basic cells

 


figure1-AND

 


figure2-FA

 


figure3-FA-AND

 


figure4-FA-NAND

 


figure5-HA-AND


 


figure6-HA-NAND

2-Layout of the multiplier core

 


Comment: DRC has been done for all Layouts above.

3-Extract and simulation of the multiplier core

3.1 Case $x=11111, y=1111111$ then $p=00000000000001$



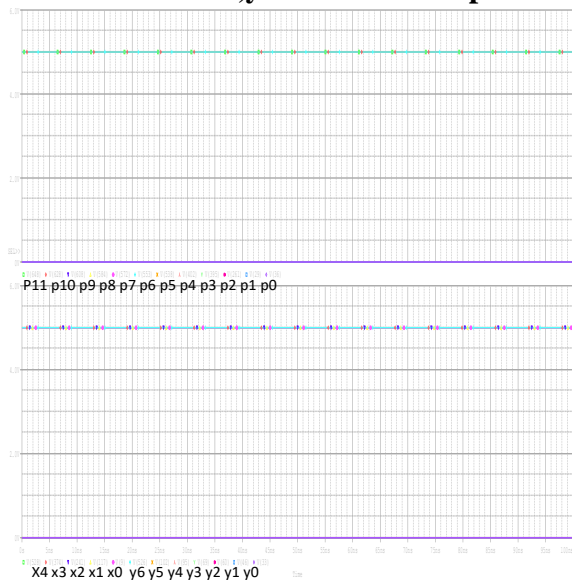3.2 Case $x=01111, y=1000000$ then $p=110001000000$




Comment: More simulation cases are given in design_simulation.doc

4-Performance estimation

 4.1 Worst Case delay calculation

P11 is the critical path: $95.31\text{n} - 50.025\text{n} = 45.285\text{ns}$



$tp_{LH} = 45.285\text{ns}$ and this is the worst case delay.

4.2 Max Frequency Calculation

$$f_{max} = \frac{1}{tp_{LH}} = \frac{1}{45.285\text{n}} = 22.082\text{ MHz}$$

4.3 Dynamic Power at max Frequency Calculation


```
l1890:
l1891:    TOTAL POWER DISSIPATION    1.26E-08  WATTS
l1892:
```

The total power dissipated is 12.6 nwatt

 4.4 Core area


$$core\ area = 1,058,414\ \lambda^2$$

5-Layout of the multiplier core after pads




6-Extract and simulation of the multiplier core After pads

 6.1 Case $x=01111, y=0111111$ then $p=001110110001$



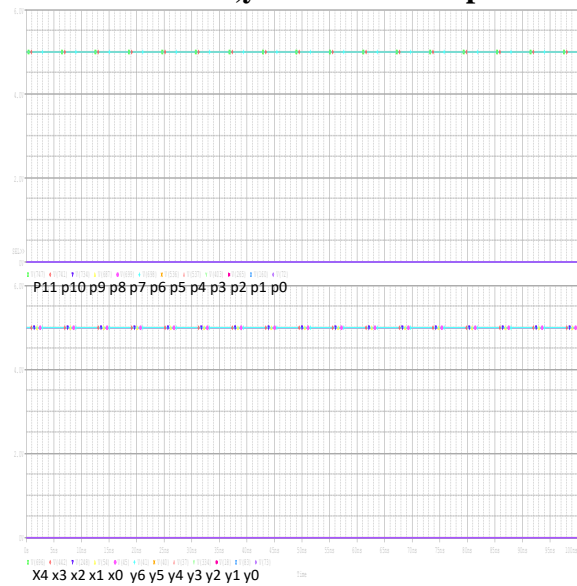6.2 Case $x=01111, y=1000000$ then $p=110001000000$




Comment: More simulation cases are given in design_simulation.doc

7-Performance estimation After pads

 7.1 Worst Case delay calculation

P11 is the critical path: $130.214n - 50.025n = 80.189ns$



$tp_{LH} = 80.189ns$ and this is the worst case delay.

7.2 Max Frequency Calculation

$$f_{max} = \frac{1}{tp_{LH}} = \frac{1}{80.189n} = 12.4705 MHz$$

7.3 Dynamic Power at max Frequency Calculation

```
25915:
25916:      TOTAL POWER DISSIPATION   7.74E-01  WATTS
25917:
```

The total power dissipated is 774 mwatt